



Potentiostat Design and Engineering

Prepared By:
Sujan Shrestha, PhD
Applications Engineer


Topics To Be Discussed

- Potentiostat Functions
- Operational Amplifiers
- Potentiostat Stability
- Current and Voltage Ranges
- Ground/Float Mode




Different Types of Power Instruments

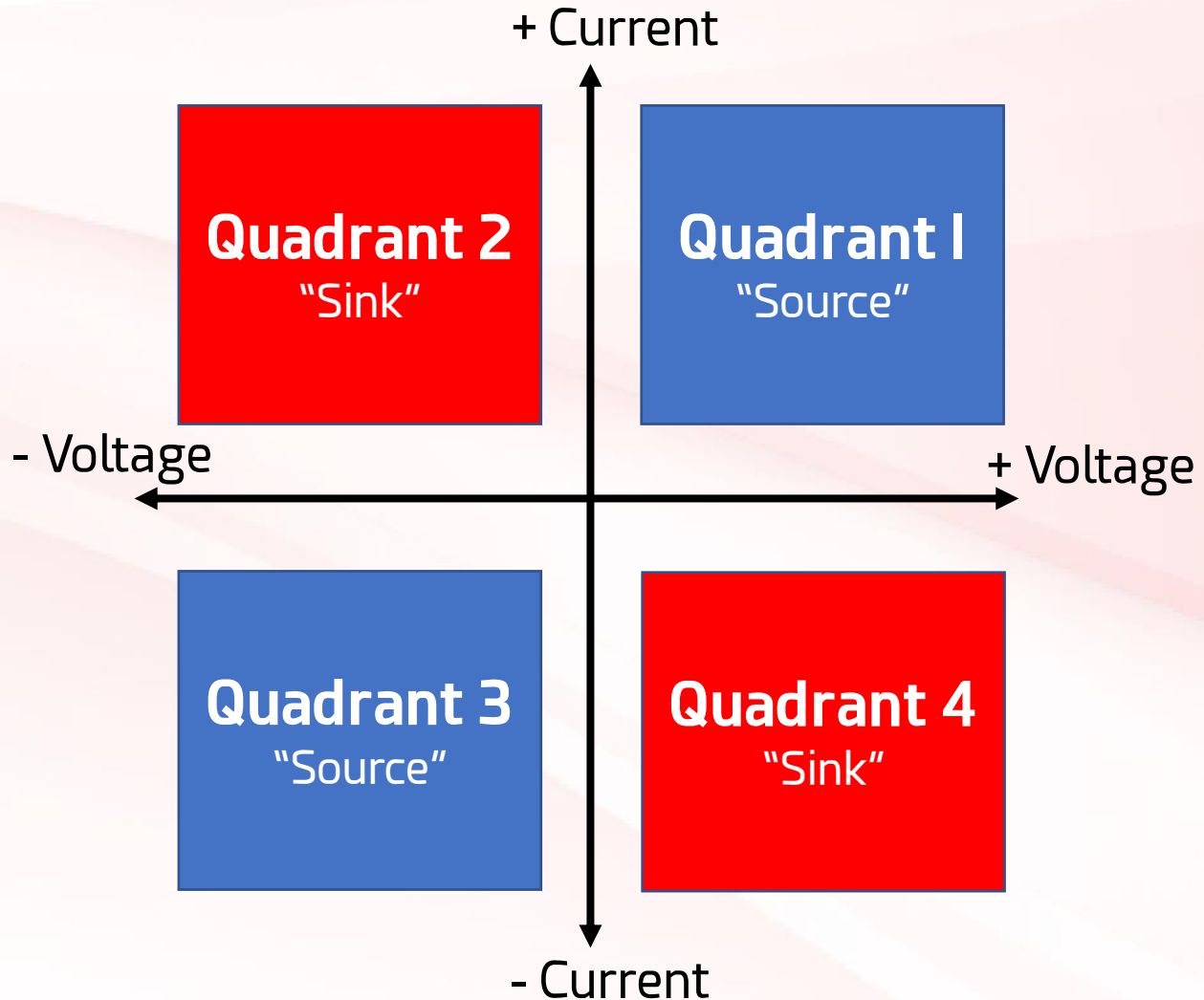- Power instruments are designed to source and/or sink power from the device under test
- Conventional power supply operate in Quadrants 1 and/or 3
- Conventional Loads operate in Quadrants 2 and/or 4
- Potentiostats and Source Measurement Units operate in all four quadrants




What is a Potentiostat?

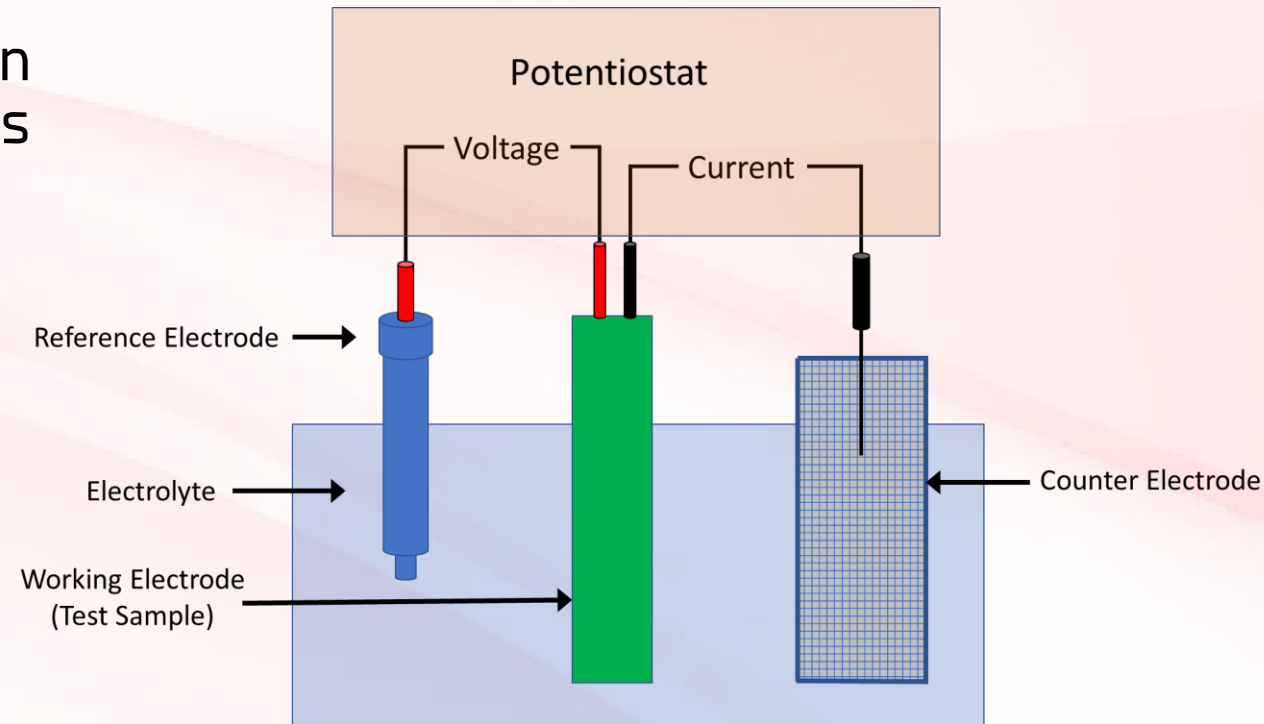- Runs 3-electrode potentiostatic experiments. Modern potentiostats run in both potentiostat and galvanostat modes
- A set voltage is applied on the Working Electrode (WE) with respect to the Reference Electrode (RE), while current flows between WE and RE
- Current does not flow through the RE
- Counter electrode can be at a different voltage than RE



Basic Functions of a Potentiostat

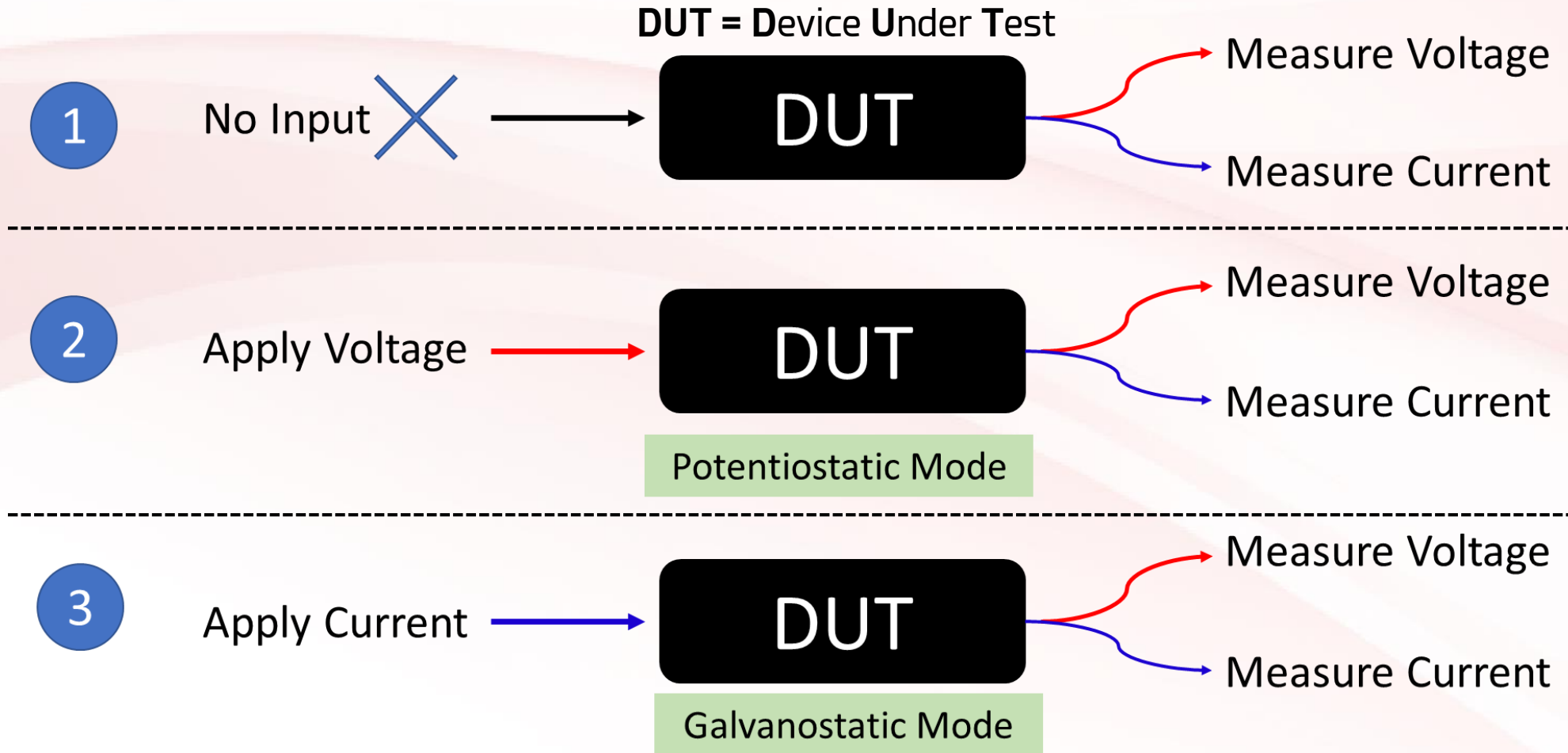


Varieties of Voltage and Current Signals


Constant Potential/Current




Pulse

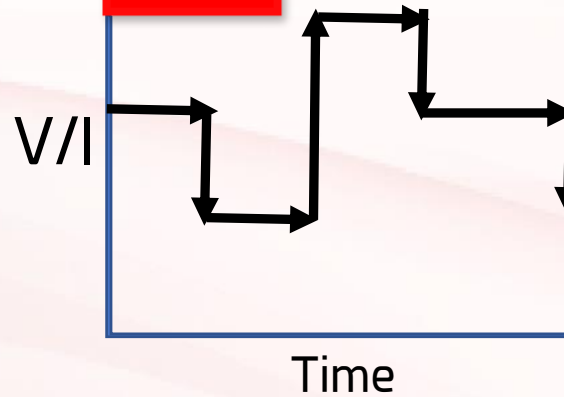


Electrochemical Impedance Spectroscopy

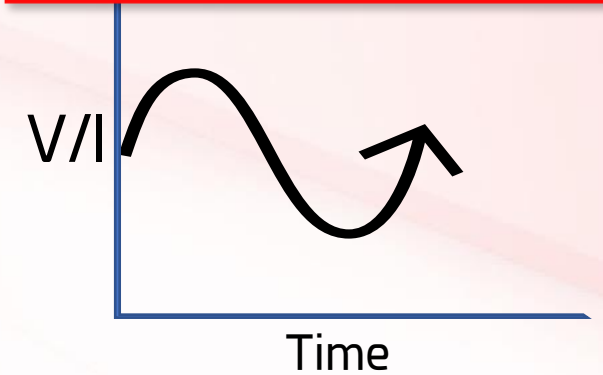

Linear Sweep Voltammetry

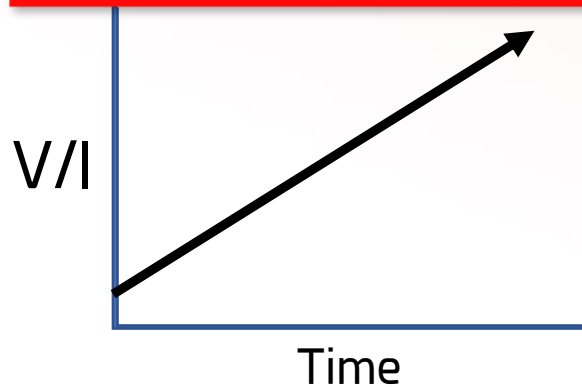


Cyclic Voltammetry



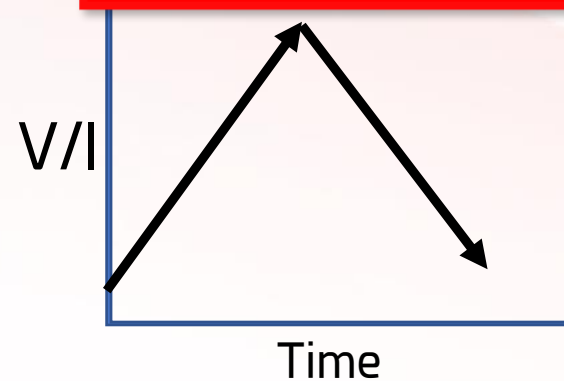


Digital Nature of Potentiostats

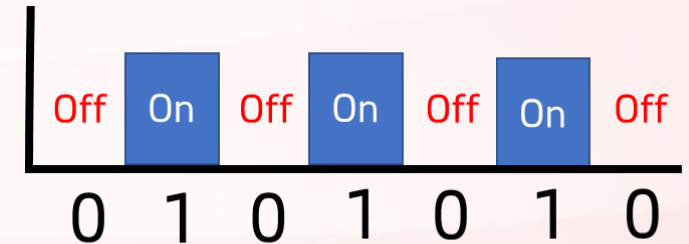
- Signals are sent and received as 0's and 1's



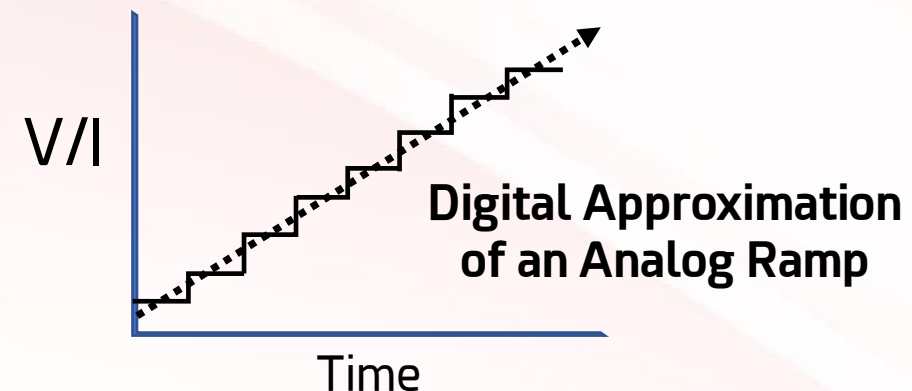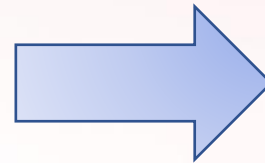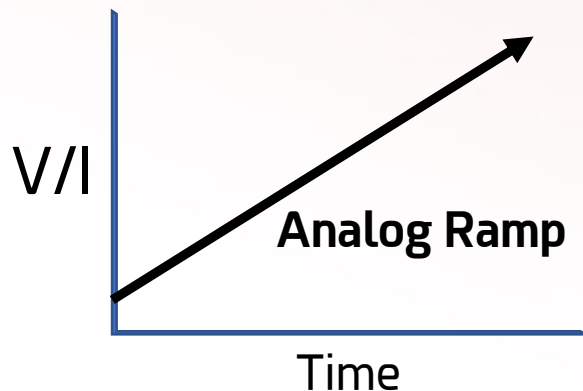- A step signal is the basic building block of all applied and received signal from the device under test



Basic Potentiostat Architecture

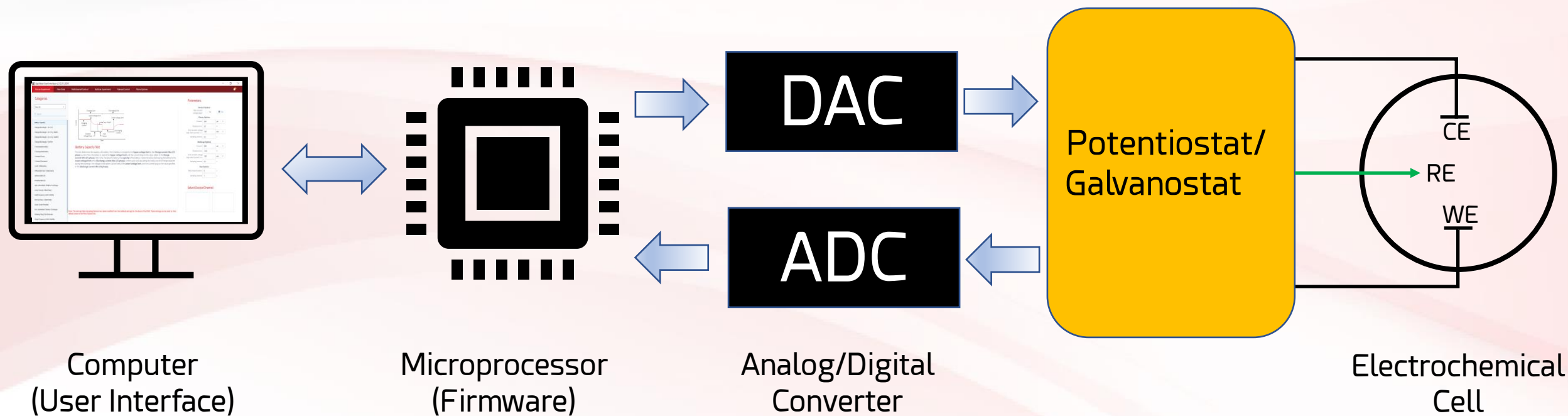


DAC = Digital to Analog Converter
ADC = Analog to Digital Converter

 Signal Flow Pathway


Ideal Operational Amplifier (Op-amps)

- Operational Amplifier (op-amps)
 - Building blocks of the potentiostat
 - "Operational" - originally used to do math operations
 - "Amplifier" - amplifies the input signal [$V_{out} = A \times (V_2 - V_1)$]
- Characteristics of an ideal op-amp
 - Open-loop gain (A_{OL}) = infinity
 - $Z_{in} = \text{infinity}$
 - $Z_{out} = 0$
 - **Response time = zero, infinite bandwidth**
 - Offset = zero ($V_{out} = 0$ if $V_2 - V_1 = 0$)

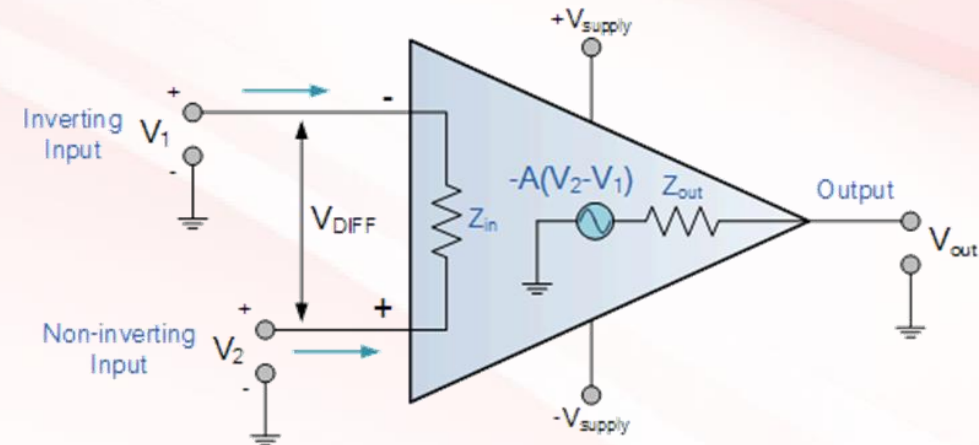


Operational Amplifier Classifications

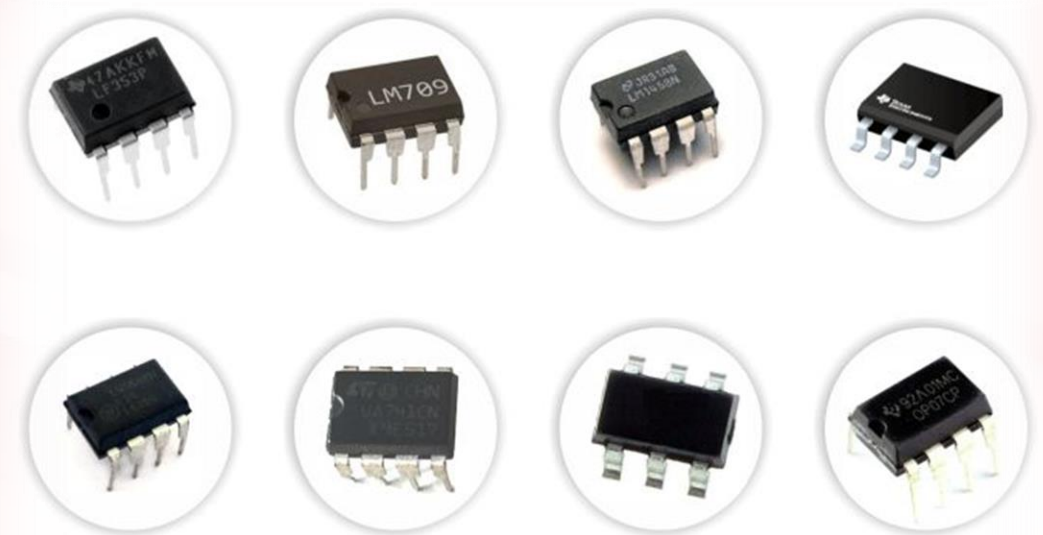- Types based on Current/Voltage input-output
 - Voltage in-Voltage out
 - Current in-Current out
 - Voltage in-Current out (Transconductance)
 - Current in-Voltage out (Transresistance)
- Types based on specifications
 - Universal
 - High resistance
 - Low temperature drift
 - High speed
 - Low power
 - High Voltage High Current
 - Programmable
- Other types
 - Differential
 - Instrumentation



Some Basic Types of Op-Amps Circuits

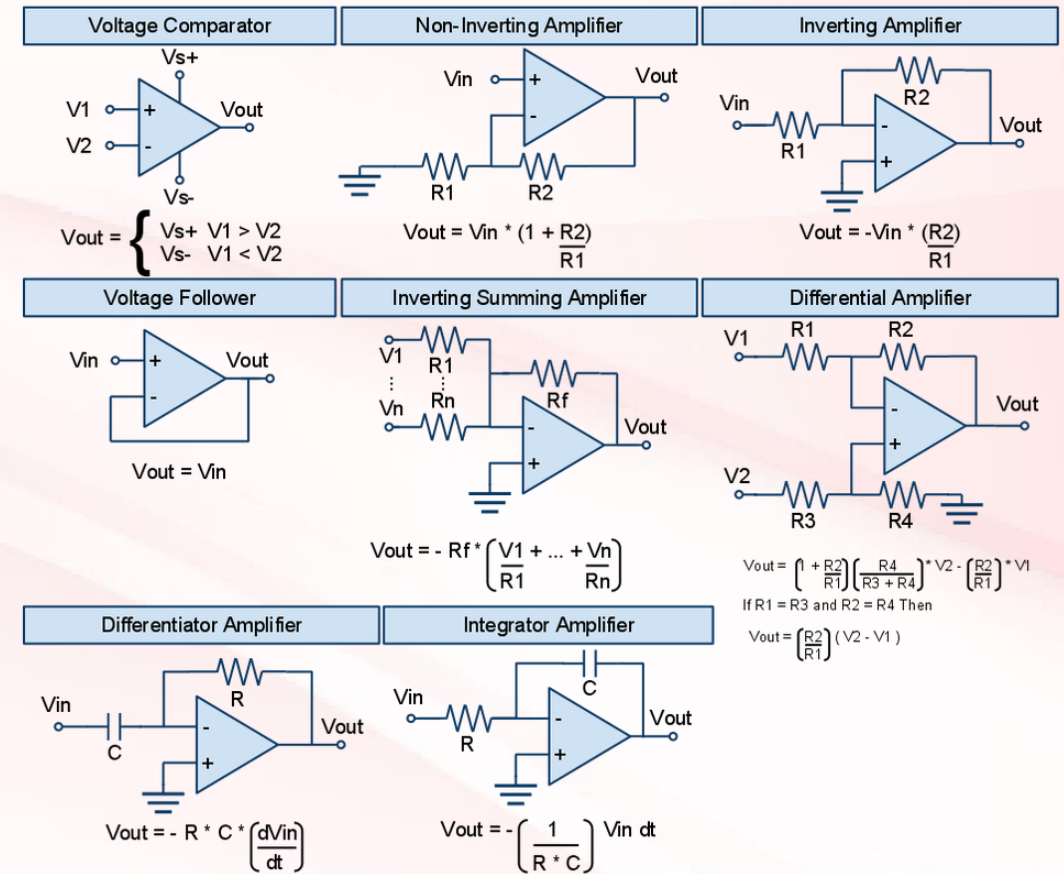
- The configuration of op-amps are limitless (logic, mathematic, filter, etc)
- Negative-feedback loop (the output is connected to the inverting input) is the most common configuration
- In fact, an op-amp is rarely used in open-loop (no feedback loop) configuration




Basic Operational Amplifier Configurations

Making Potentiostats Using Op-Amps

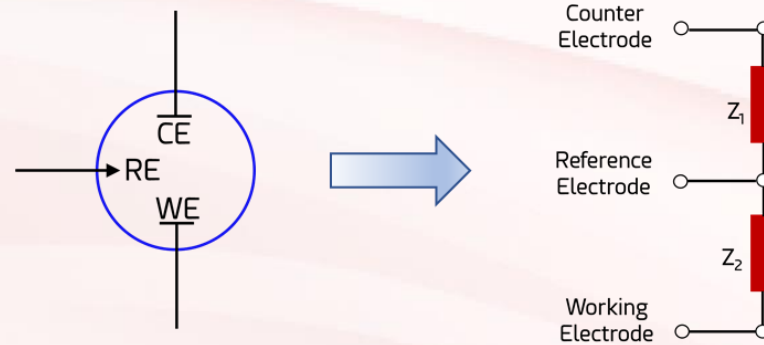- An electrochemical cell can be simulated with resistors and capacitors



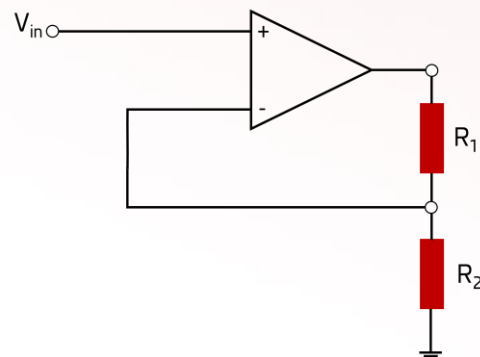
- A simple potentiostat can be created using one of the basic op-amp circuits



Non-inverting Amplifier





Remove
 R_1 and R_2

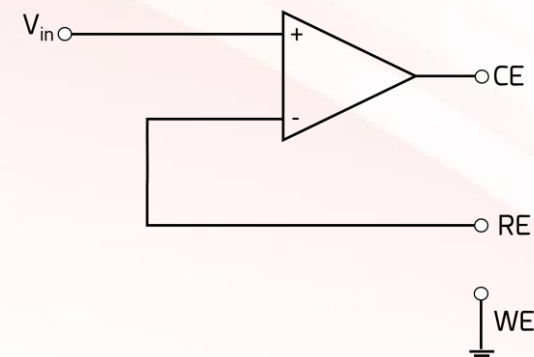

A Simple Potentiostat


A Real Potentiostat is Complex!

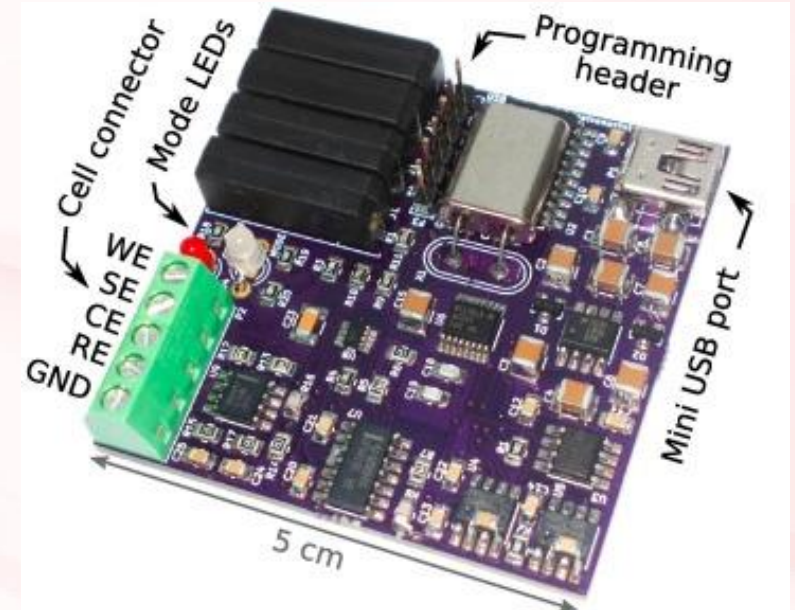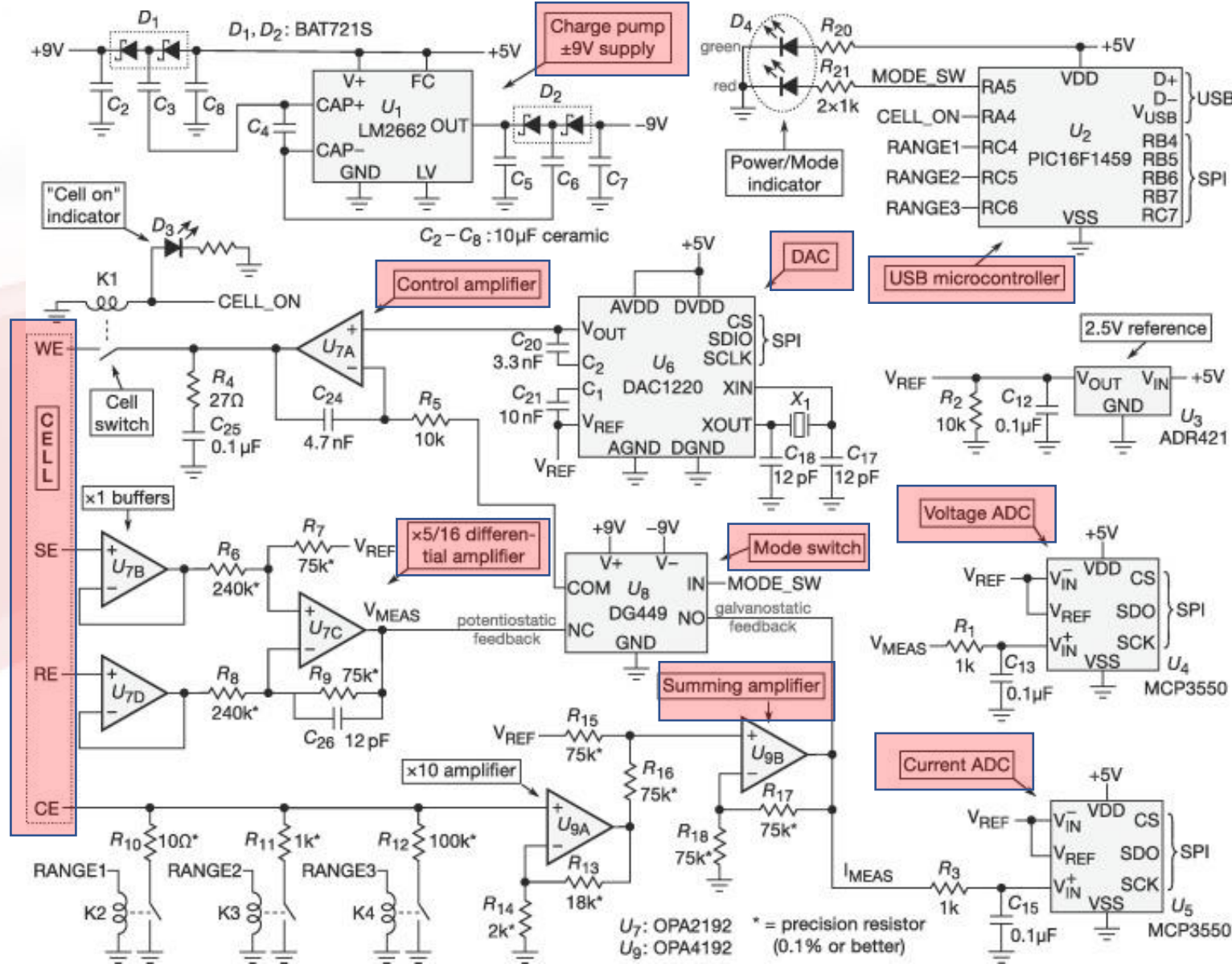

"A USB-controlled potentiostat/galvanostat for thin-film battery characterization"


Dobbelaere, et al. Hardware X 2 (2017) 34-49

Simplified Potentiostat Design

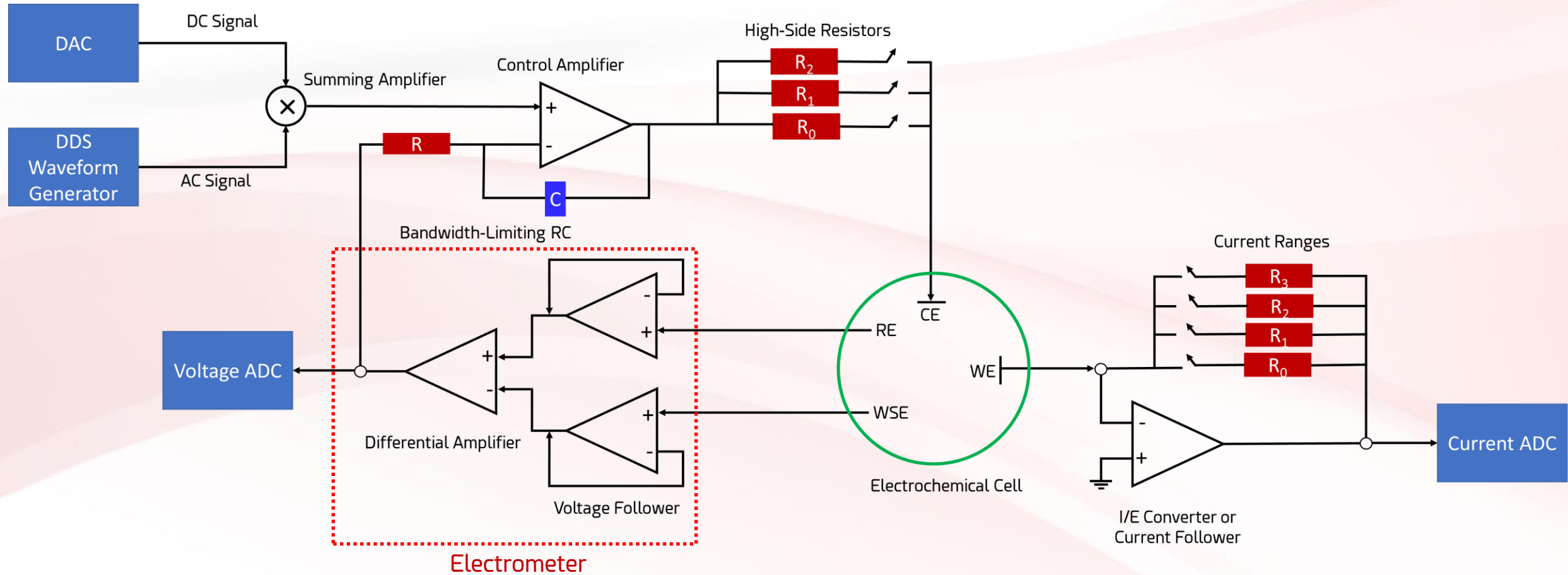


DAC = Digital to Analog Converter
ADC = Analog to Digital Converter
DDS = Direct Digital Synthesizer

Simplified Galvanostat Design

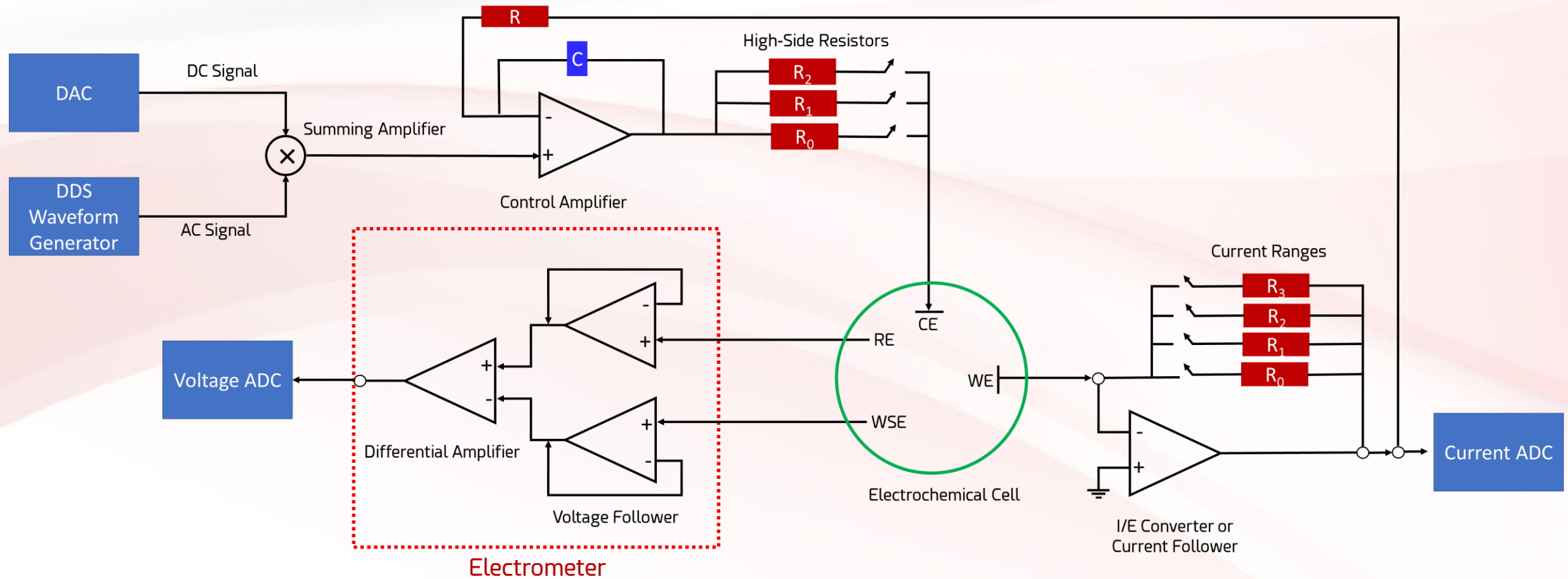


Open-Loop Gain vs Closed-Loop Gain

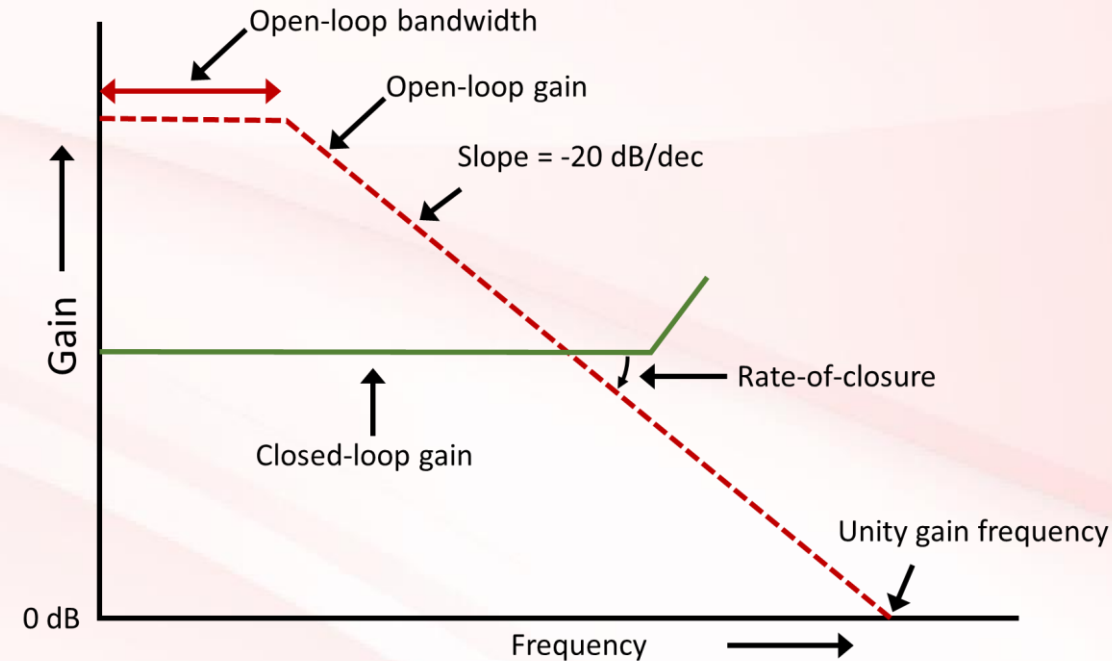- The gain of real op-amp is frequency dependent
- Closed-loop amplifier circuit cannot supply more gain at higher frequencies than available
 - Closed-loop is when a feedback loop exists
- The angle between closed-loop gain and open-loop gain is called the rate-of-closure, which determines stability of the circuit




Stability Criteria


- The rate-of-closure determines if the circuit will be stable or not

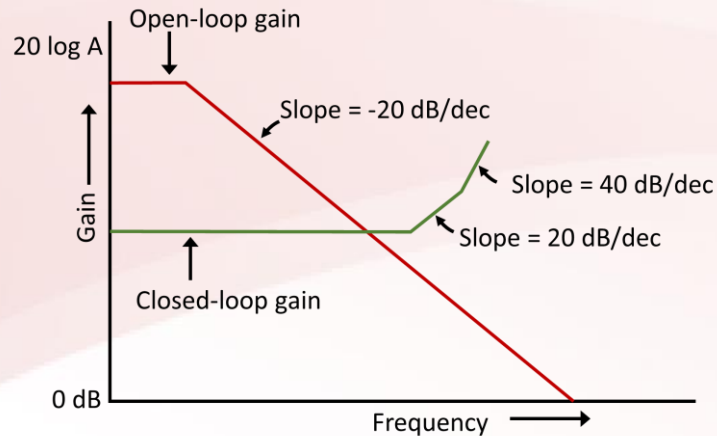

Condition 1: Optimal stability
Rate-of-Closure < 40 DB

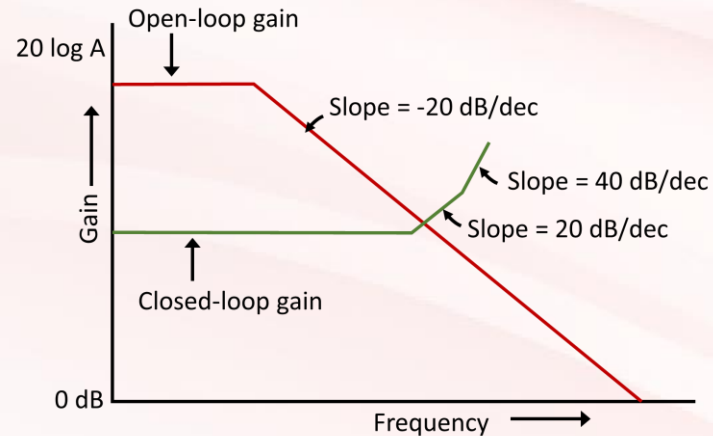

Condition 2: Marginal stability
Rate-of-Closure = 40 DB


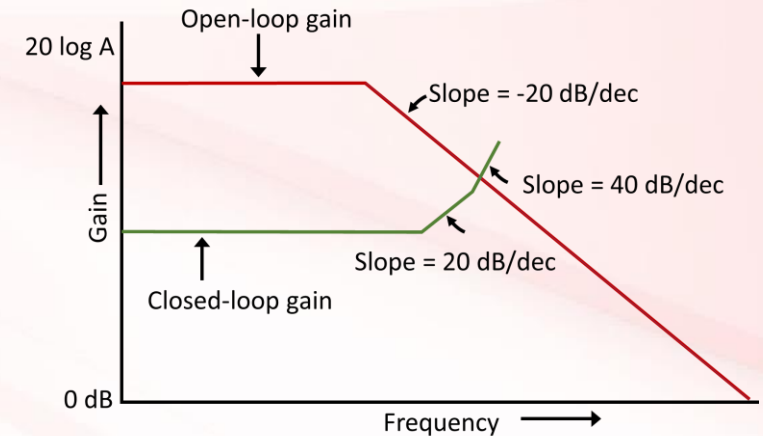


Condition 3: Instability
Rate-of-Closure > 40 DB

- Rate-of-closure can be controlled by modulating the bandwidth of the control amplifier


Potentiostat Stability: *Bandwidth Index*

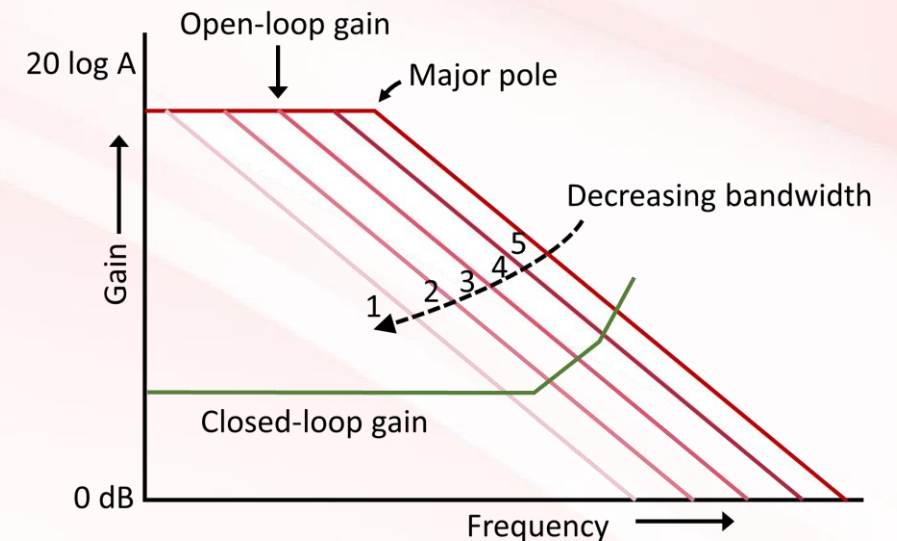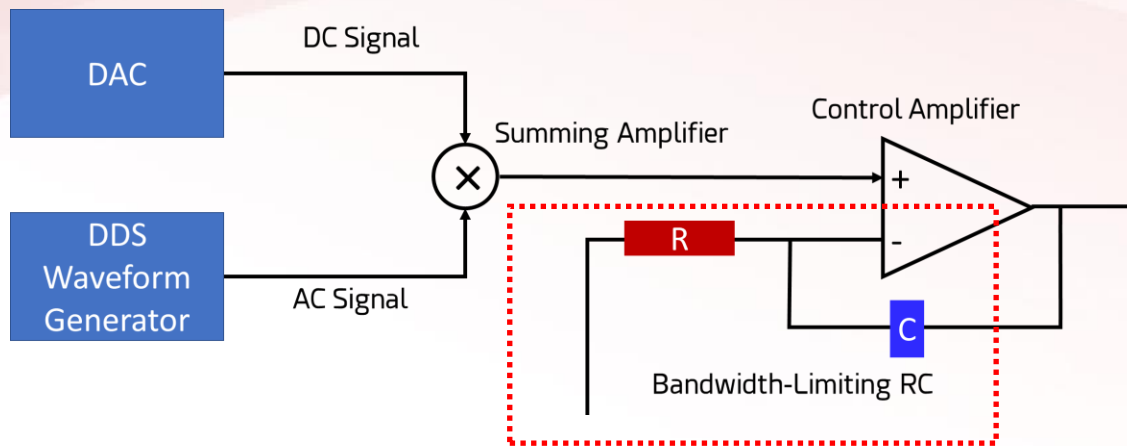- Potentiostat stability can be controlled by varying bandwidth-limiting RC
- This is labeled as ***Bandwidth Index*** in the Squidstat User Interface software




Potentiostat Stability: *Stability Factor*

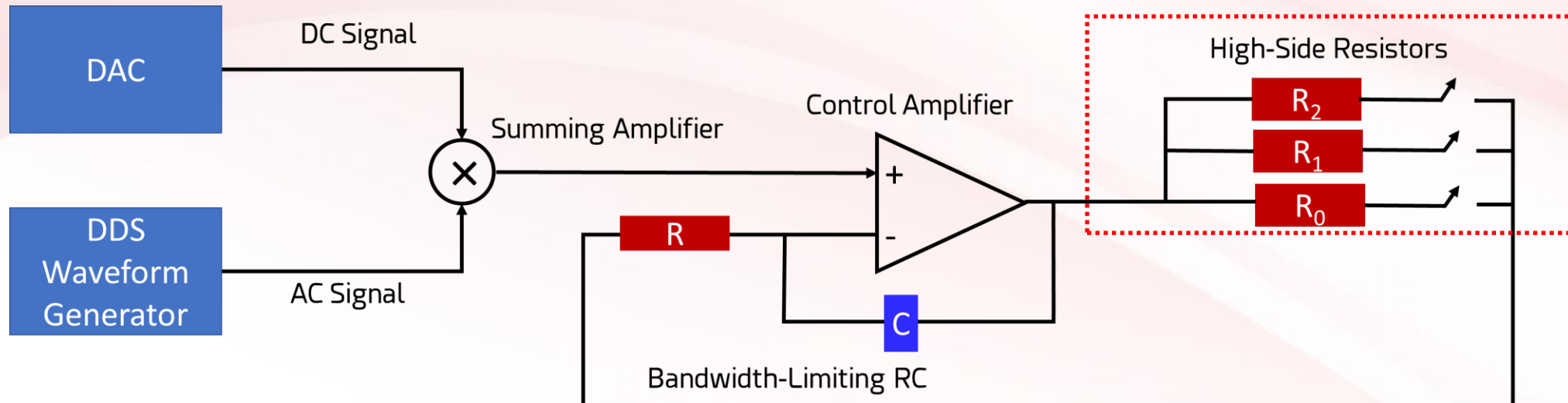- The high-side resistors also control the bandwidth of the control amplifier, but do so in a less predictable way than the bandwidth-limiting RC




Current Measurement

- In most potentiostats, current is measured by measuring the voltage drop across a resistor
 - $V_{out} = IR_x$, where $x = 0,1,2...N$
 - N is the number of ranges
- If the max voltage drop across each resistor is 1 V...
 - For $R = 10\ \Omega$, Range = 0.1 A or 100 mA
 - For $R = 100\ \Omega$, Range = 0.01 A or 10 mA
- Resistor precision determines the current measurement accuracy
- Current ranging
 - Auto-range: the software/firmware selects the best resistor for accuracy
 - Fixed-range: the user selects the resistor

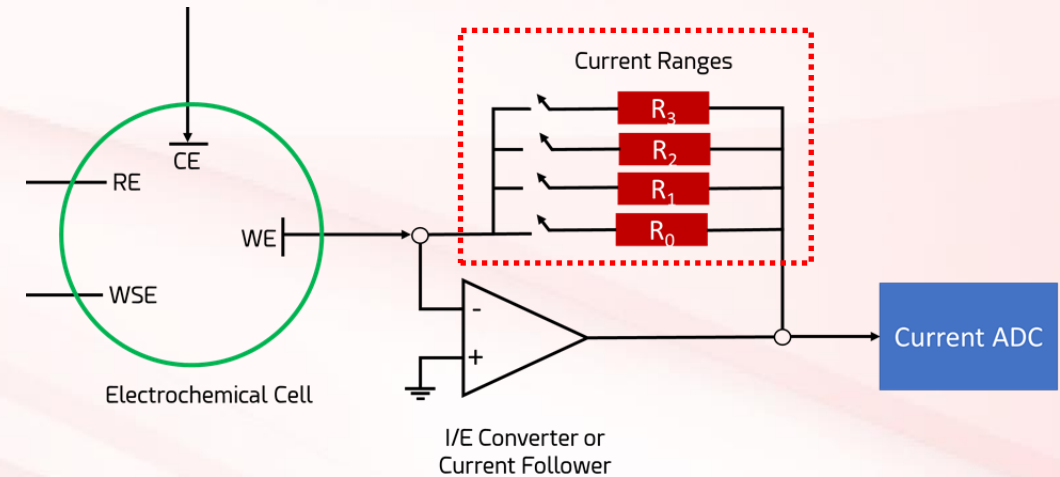


Voltage and Current Ranges

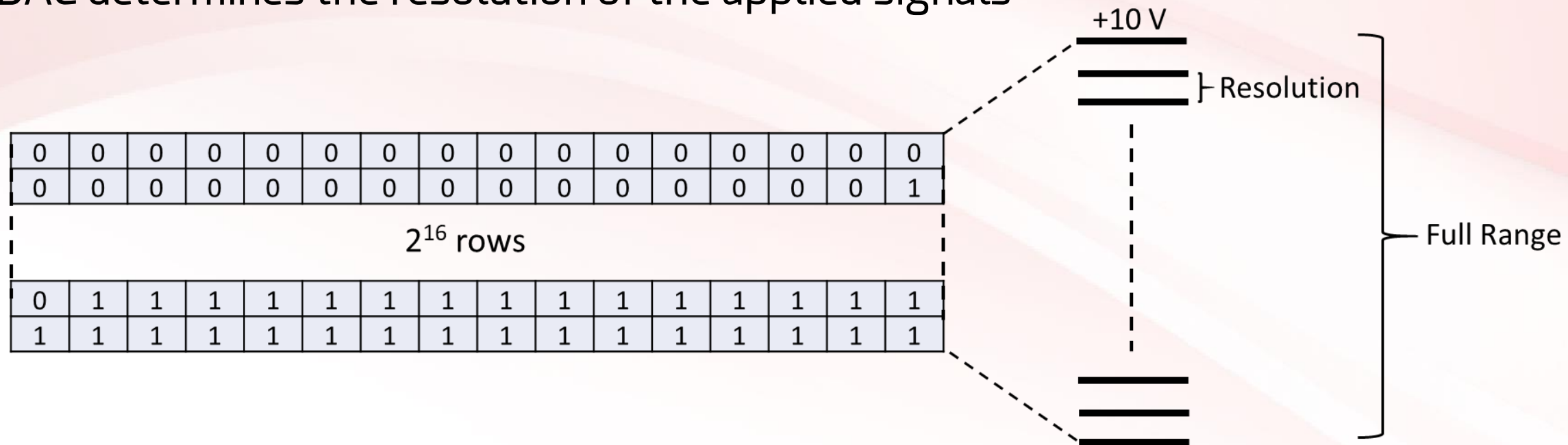- ADC determines the resolution of the measured signal
 - 16-bit ADC means there are 2^{16} binary numbers to represent a voltage or current range
- DAC determines the resolution of the applied signals




Ground Loops

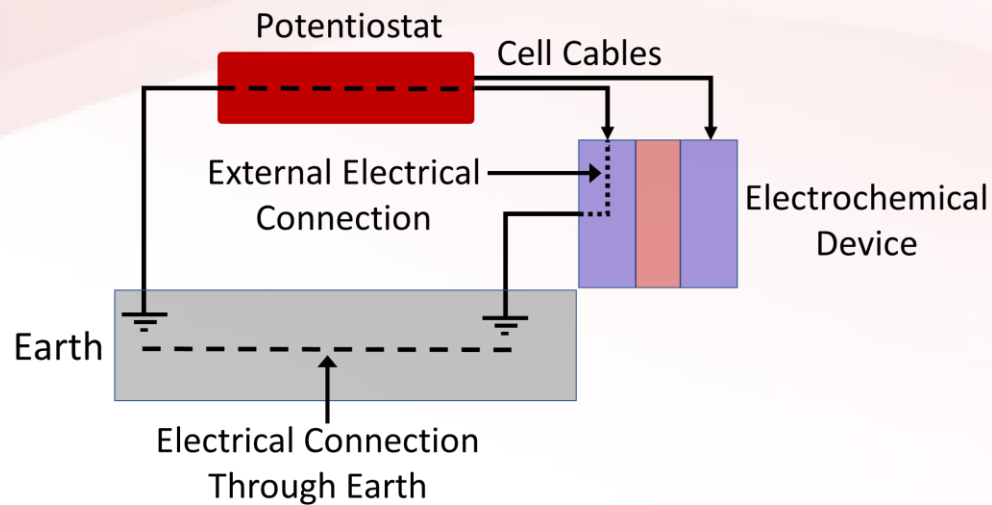- "Ground" acts as a voltage reference point and current sink
- A ground loop occurs when two or more instrument are connected via "ground"
- A ground loop introduces noise and instability



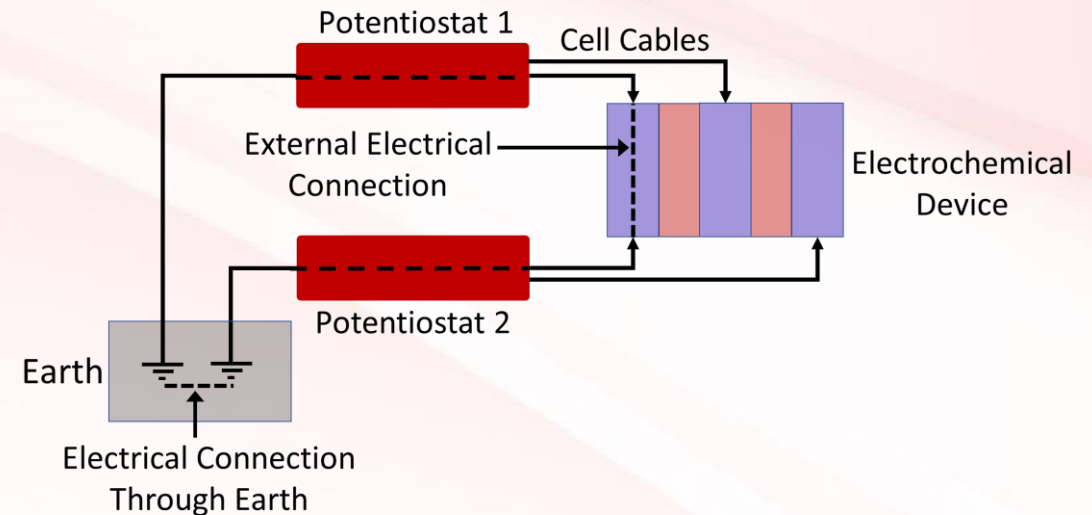
Ground Loop Through a Grounded Electrochemical Device




Two Potentiostats In Ground Loop Through Common Connection

Floating Mode

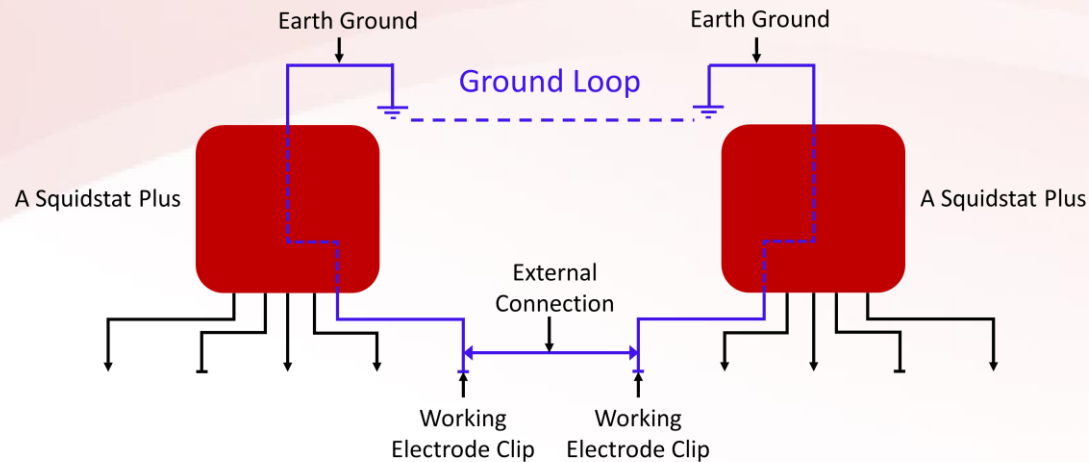- When an instrument is disconnected from "Ground", it is in a floating mode



Ground Mode

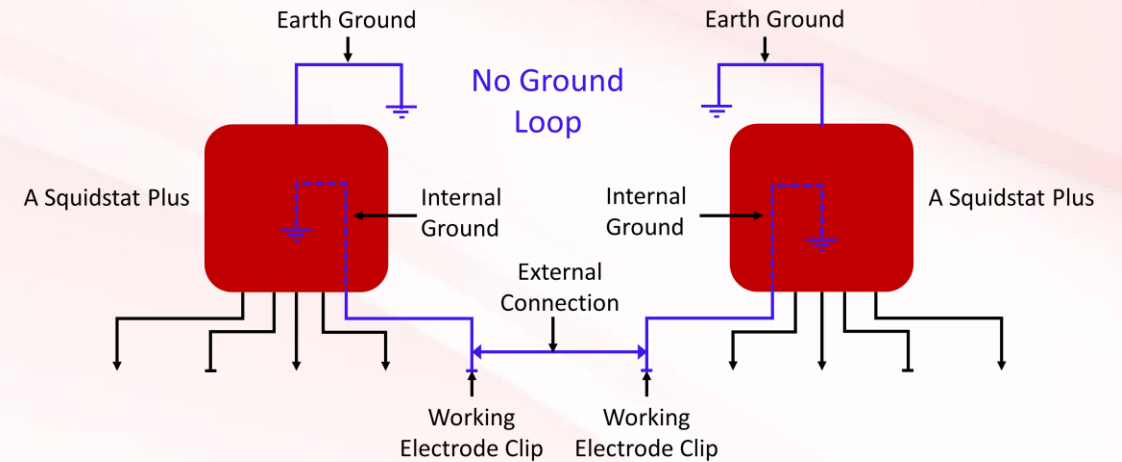

Float Mode


Some Final Points to Consider

- Noise management
 - Thermal noise
 - Atmospheric noise
 - Shot noise
 - Flicker noise
 - Burst noise
 - Transit-time noise
 - Filter
- Issues caused by digital approximation of analog signals
- Data sampling

Thermal Noise

$$E = (4 R k T \Delta F)$$

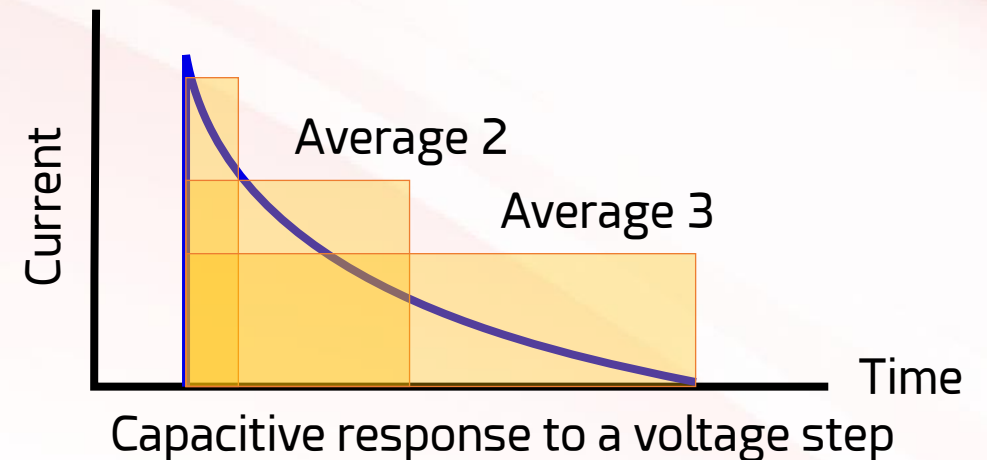E is RMS noise in voltage
R is resistance
k is Boltzmann's constant
T is temperature
 ΔF is frequency range



FORWARD-THINKING HARDWARE. INTUITIVE SOFTWARE.

We're Devoted to Making Your Job **EASIER**



Sujan Shrestha, PhD

Applications Engineer

sujan@admiralinstruments.com

Office: +1 480 256 8706

Follow @potentiostats



AdmiralInstruments.com



*Making the next generation of electrochemistry
instruments **truly accessible worldwide***